

Introduction to Electrical Engineering

Aakash Jog

2014-15

Contents

1	Instructor Information	2
I		3
1		3
	Recitation 1 – Exercise 1.	3
	Recitation 1 – Solution 1.	3
	Recitation 1 – Exercise 2.	4
	Recitation 1 – Solution 2.	4
	Recitation 1 – Exercise 3.	5
	Recitation 1 – Solution 3.	5



This work is licensed under the Creative Commons Attribution-NonCommercial-ShareAlike 4.0 International License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-nc-sa/4.0/>.

1 Instructor Information

Naftali Landsberg

Telephone: +972 3-640-6422


Mobile: +972 54-429-3212

E-mail: naftali.landsberg@gmail.com

Part I

1

Recitation 1 – Exercise 1.

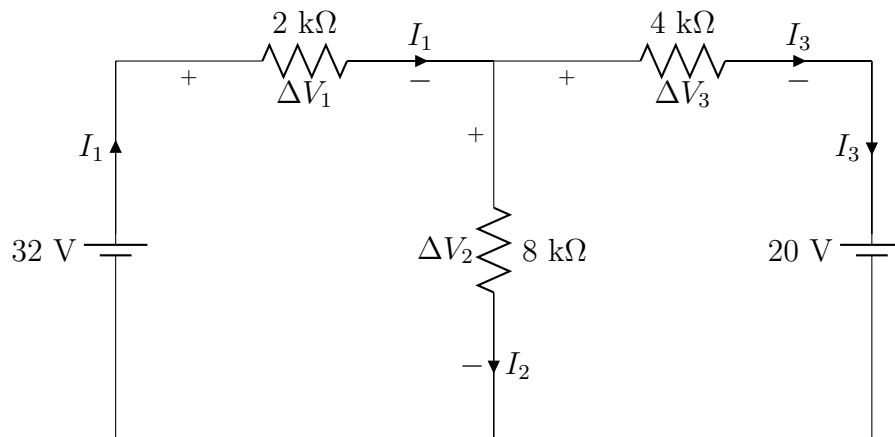

Recitation 1 – Solution 1.

By KCL for the upper junction,

$$I_1 - I_2 - I_3 = 0$$

By KCL for the lower junction,

$$-I_1 + I_2 + I_3 = 0$$

By KVL for left loop,

$$-32 + \Delta V_1 + \Delta V_2 = 0$$


By KVL for right loop,

$$-20 - \Delta V_2 + \Delta V_3 = 0$$

By KVL for the larger loop,

$$32 - \Delta V_1 - \Delta V_2 - 20 = 0$$

Recitation 1 – Exercise 2.

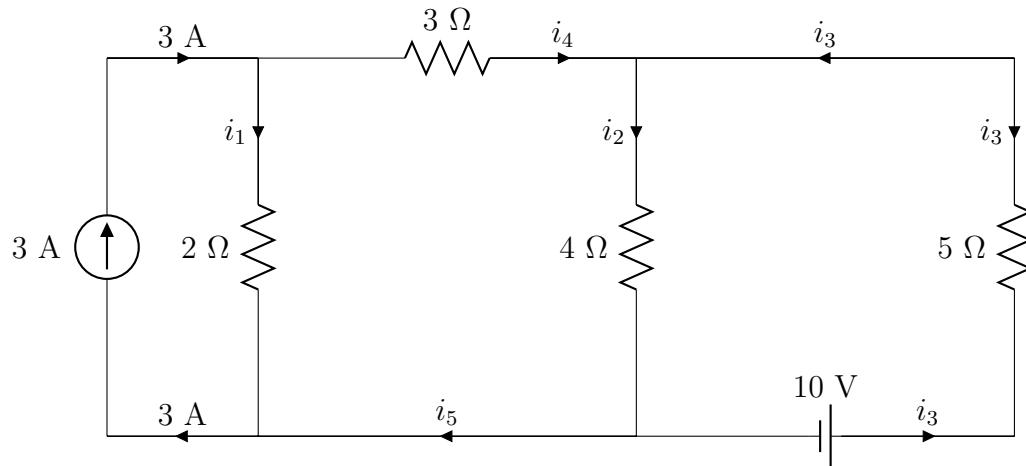

Recitation 1 – Solution 2.

By KCL at 2,

$$3 - i_1 - i_4 = 0$$

By KCL at 3,

$$i_4 + i + 3 + i_2 = 0$$

By KCL at 6,

$$-i_3 - i_2 - i_5 = 0$$

By KCL at 7,

$$i_5 + i_1 - 3 = 0$$

By KVL in loop A,

$$2i_1 - V_x = 0$$


By KVL in loop B,

$$3i_4 - 4i_2 - 2i_1 = 0$$

By KVL in loop C,

$$-5i_3 + 10 + 4i_2 = 0$$

Recitation 1 – Exercise 3.

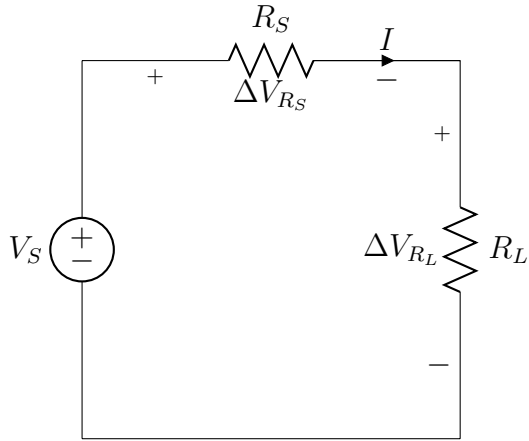

Find R_L so that it would have maximum available power.

Recitation 1 – Solution 3.

By KVL,

$$\begin{aligned}\Delta V_{R_S} + \Delta V_{R_L} - V_S &= 0 \\ \therefore \Delta V_{R_S} + \Delta V_{R_L} &= V_S \\ IR_S + IR_L &= V_S \\ \therefore I &= \frac{V_S}{R_S + R_L} \\ P_L &= I^2 R_L \\ &= \left(\frac{V_S}{R_S + R_L} \right)^2 R_L\end{aligned}$$

The power is maximum if $\frac{dP_L}{dR_L} = 0$.

Therefore, differentiating and maximizing, P_L is maximum if $R_L = R_S$.

Therefore,

$$\begin{aligned}P_{L\max} &= \frac{V_S^2}{(2R_S)^2} \cdot R_S \\ &= \frac{V_S^2}{4R_S}\end{aligned}$$