

Introduction to Electrical Engineering

Aakash Jog

2014-15

Contents

1	Lecturer Information	2
2	Required Reading	2
I	Basic Definitions and Laws	3
1	Basic Definitions	3
2	Kirchoff's Laws	3
2.1	Kirchoff's Current Law	3
2.2	Kirchoff's Voltage Law	4
3	Components	5
3.1	Resistors	5
3.1.1	Linear Time Independent Resistor	5
3.1.2	Non-linear Resistors (Diodes)	6
3.2	Independent Sources	7
3.2.1	Voltage Sources	7
3.2.2	Current Sources	8
3.2.3	Real Batteries	9

1 Lecturer Information

Prof. Moshe Tur

Office: Wolfson 413

Telephone: 03-640-8125

E-mail: tur@post.tau.ac.il

2 Required Reading

C.A. Desoer and E.S. Kuh: *Basic Circuit Theory*, Mc-Graw-Hill, International Edition.

Part I


Basic Definitions and Laws

1 Basic Definitions


Definition 1 (Electrical circuit). A collection of interconnected components.

Definition 2 (Lumped component). An electrical component whose dimensions are very very small compared to the wavelength of the electromagnetic waves passing through it is called a lumped component.

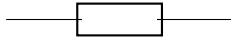Definition 3 (One port device). An electrical component with two terminals is called a one port device.



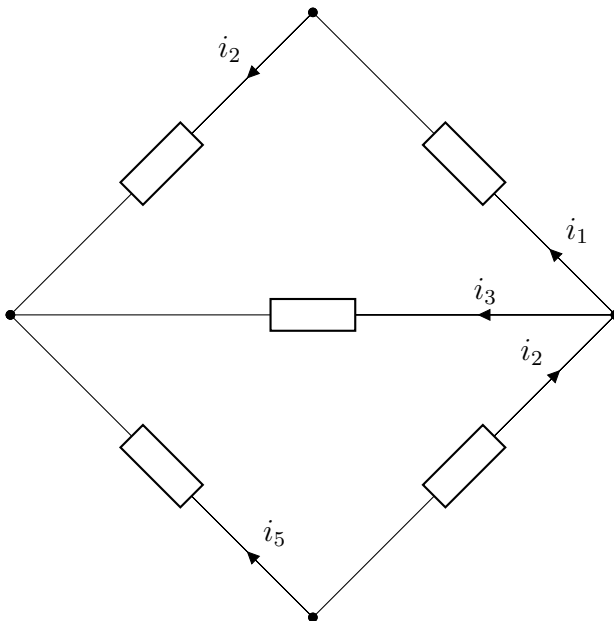
Definition 4 (Nodes and branches). In the figure, all the black dots are called nodes. The parts of the circuit between two nodes are called branches.



2 Kirchoff's Laws

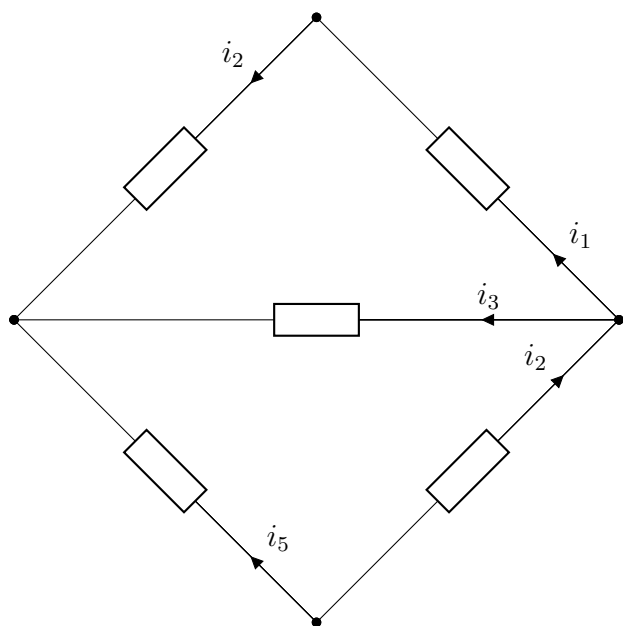2.1 Kirchoff's Current Law


The sum of all currents entering or exiting a node is zero.



$$i_1 + i_3 - i_4 = 0$$

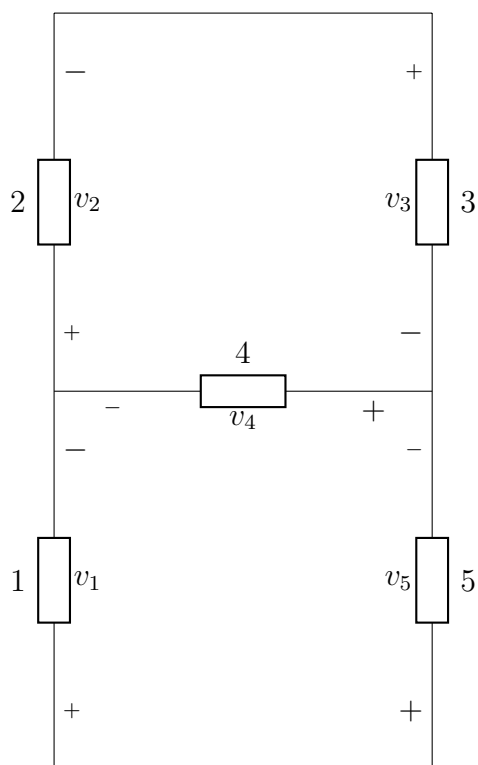2.2 Kirchhoff's Voltage Law

The sum of all branch voltages along a closed loop is zero.



$$v_1 - v_4 - v_5 = 0$$

$$v_2 + v_3 + v_4 = 0$$


$$v_1 + v_2 + v_3 - v_5 = 0$$


3 Components

3.1 Resistors

Definition 5 (Resistor). A two terminal component is called a resistor if the voltage across it at any given time t is a function of the current at the same time t .

3.1.1 Linear Time Independent Resistor

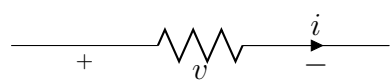

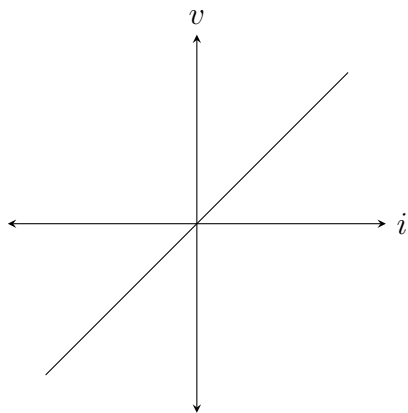


$$v(t) = R \cdot i(t)$$

$$i(t) = G \cdot v(t)$$

R is called the resistance and G is called the conductance.

3.1.2 Non-linear Resistors (Diodes)

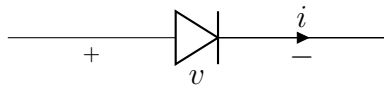

$$i(t) = I_s \left(e^{\frac{q \cdot v(t)}{kT}} - 1 \right)$$


I_s = reverse current

k = Boltzman constant

T = absolute temperature

q = electronic charge

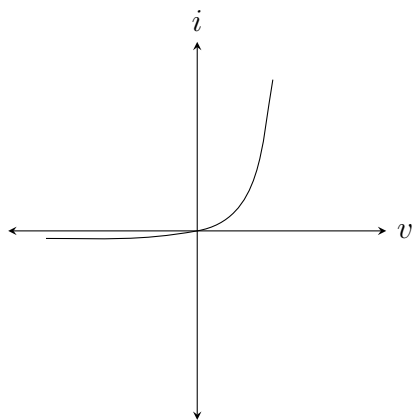
$$\frac{kT}{q} = 0.026 \text{ (at 300K)}$$




3.2 Independent Sources

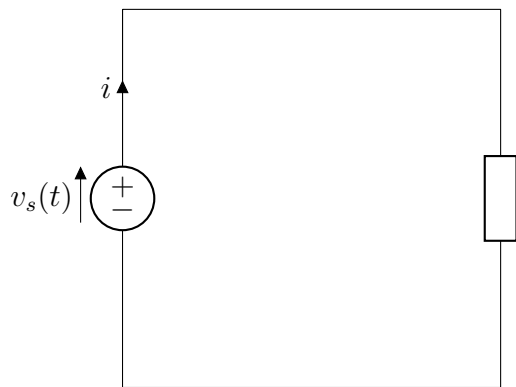3.2.1 Voltage Sources



Definition 6 (Voltage source). A two terminal component is called a voltage source if the voltage on its terminals is independent of the current through it.




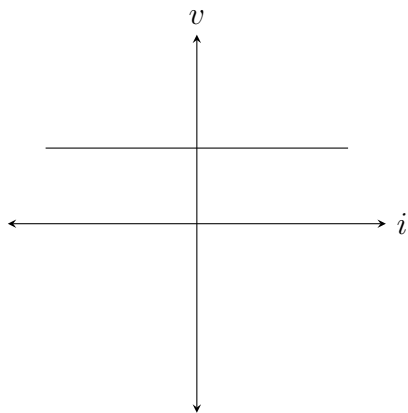


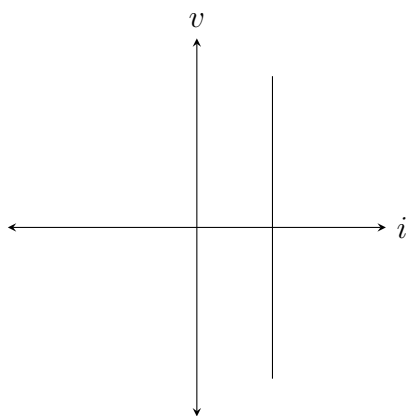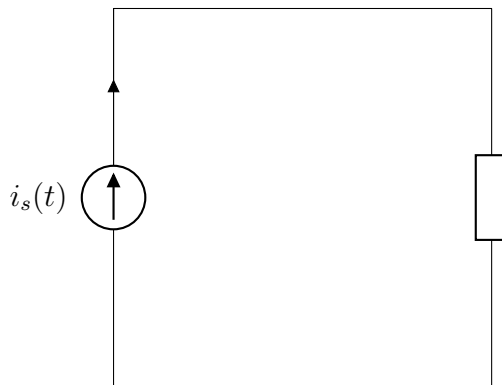3.2.2 Current Sources

Definition 7 (Current source). A two terminal component is called a current source if it can supply a current $i_s(t)$ independent of the voltage across its terminals.



3.2.3 Real Batteries

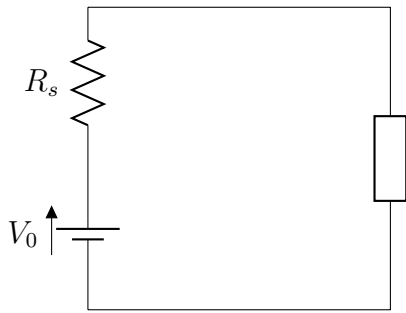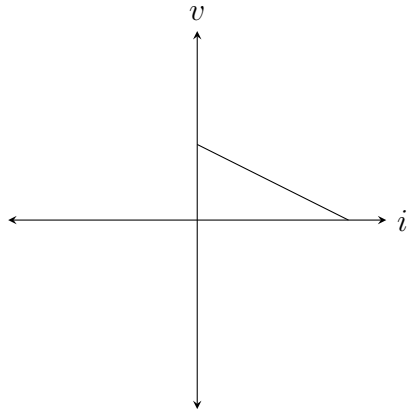

$$\begin{aligned}0 &= -V_0 + v_R + v \\v &= V_0 - v_R \\ \therefore v &= V_0 - R_s i\end{aligned}$$