

Introduction to Electrical Engineering

Aakash Jog

2014-15

Contents

1	Lecturer Information	3
2	Required Reading	3
I	Basic Definitions and Laws	4
1	Basic Definitions	4
2	Kirchoff's Laws	4
2.1	Kirchoff's Current Law	4
2.2	Kirchoff's Voltage Law	5
3	Components	6
3.1	Resistors	6
3.1.1	Linear Time Independent Resistor	6
3.1.2	Non-linear Resistors (Diodes)	7
3.2	Independent Sources	8
3.2.1	Voltage Sources	8
3.2.2	Current Sources	9
3.2.3	Real Batteries	10
3.3	Capacitor	10
3.3.1	Linear Capacitors	10
3.4	Inductor	11

4	Waveforms	12
4.1	DC (Constant Function)	12
4.2	Sinusoidal Wave	12
4.3	Step Function	13
4.4	Rectangular Pulse	13
4.5	Dirac δ function	14
4.6	Ramp Function	15
4.7	Doublet Function	15
4.8	Relation Between Standard Waveforms	15
5	Power and Energy	16
5.1	Energy Stored in a Capacitor	17
5.2	Energy Stored in an Inductor	17
II	Simple Circuits	17
1	Equivalent Circuits	18

1 Lecturer Information

Prof. Moshe Tur

Office: Wolfson 413

Telephone: 03-640-8125

E-mail: tur@post.tau.ac.il

2 Required Reading

C.A. Desoer and E.S. Kuh: *Basic Circuit Theory*, Mc-Graw-Hill, International Edition.

Part I


Basic Definitions and Laws

1 Basic Definitions


Definition 1 (Electrical circuit). A collection of interconnected components.

Definition 2 (Lumped component). An electrical component whose dimensions are very very small compared to the wavelength of the electromagnetic waves passing through it is called a lumped component.

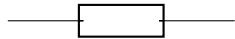Definition 3 (One port device). An electrical component with two terminals is called a one port device.



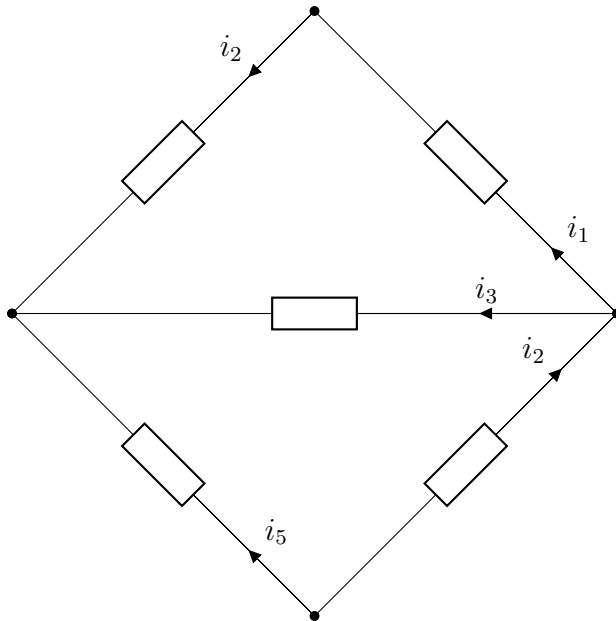
Definition 4 (Nodes and branches). In the figure, all the black dots are called nodes. The parts of the circuit between two nodes are called branches.



2 Kirchhoff's Laws

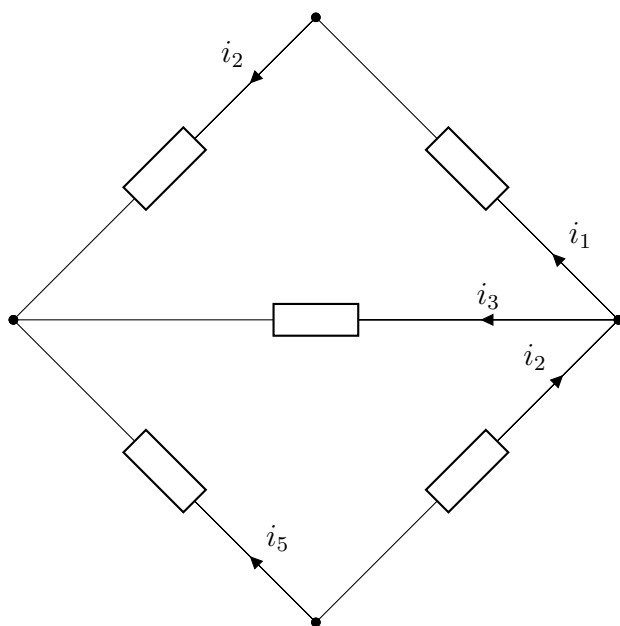2.1 Kirchhoff's Current Law


The sum of all currents entering or exiting a node is zero.



$$i_1 + i_3 - i_4 = 0$$

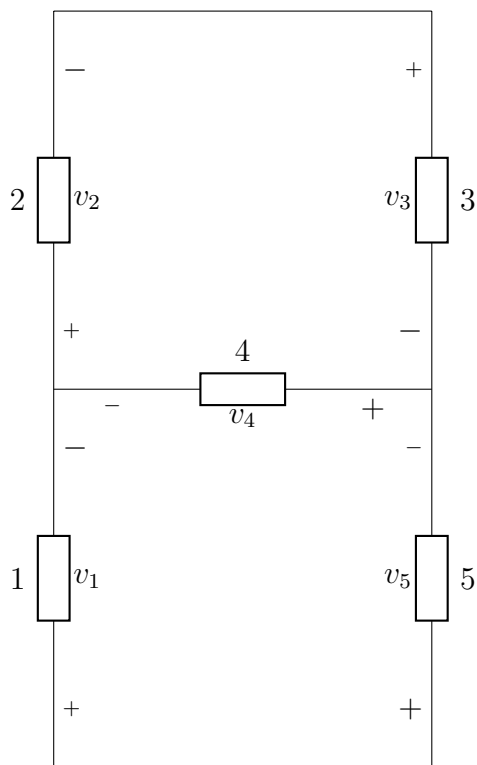2.2 Kirchoff's Voltage Law

The sum of all branch voltages along a closed loop is zero.




$$\begin{aligned} v_1 - v_4 - v_5 &= 0 \\ v_2 + v_3 + v_4 &= 0 \\ v_1 + v_2 + v_3 - v_5 &= 0 \end{aligned}$$


3 Components

3.1 Resistors

Definition 5 (Resistor). A two terminal component is called a resistor if the voltage across it at any given time t is a function of the current at the same time t .

3.1.1 Linear Time Independent Resistor

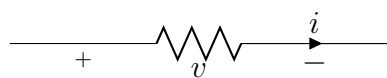

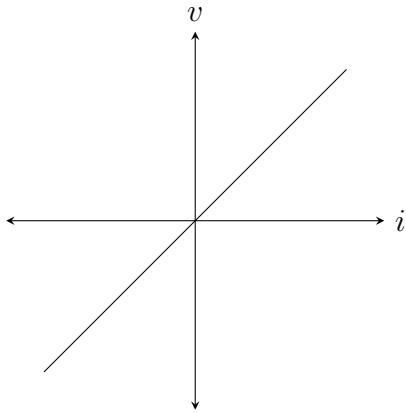


$$v(t) = R \cdot i(t)$$

$$i(t) = G \cdot v(t)$$

R is called the resistance and G is called the conductance.

3.1.2 Non-linear Resistors (Diodes)

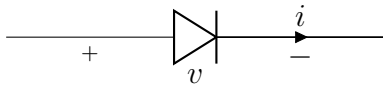

$$i(t) = I_s \left(e^{\frac{q \cdot v(t)}{kT}} - 1 \right)$$


I_s = reverse current

k = Boltzman constant

T = absolute temperature

q = electronic charge

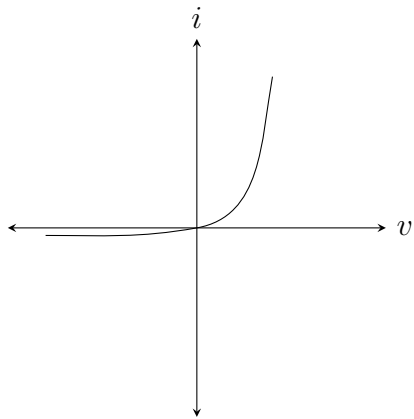
$$\frac{kT}{q} = 0.026 \text{ (at 300K)}$$




3.2 Independent Sources

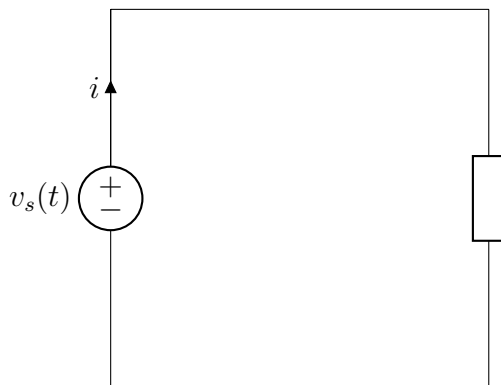3.2.1 Voltage Sources



Definition 6 (Voltage source). A two terminal component is called a voltage source if the voltage on its terminals is independent of the current through it.




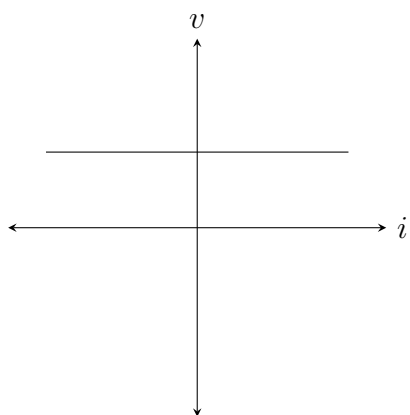


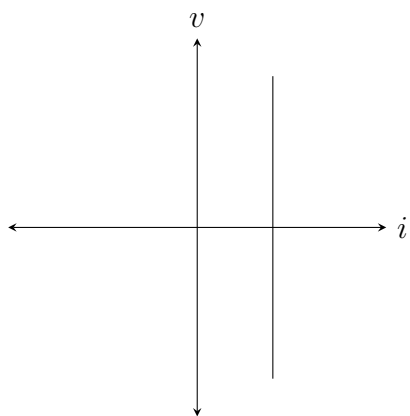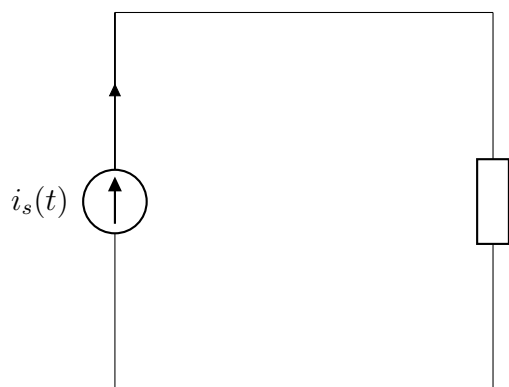3.2.2 Current Sources

Definition 7 (Current source). A two terminal component is called a current source if it can supply a current $i_s(t)$ independent of the voltage across its terminals.




3.2.3 Real Batteries

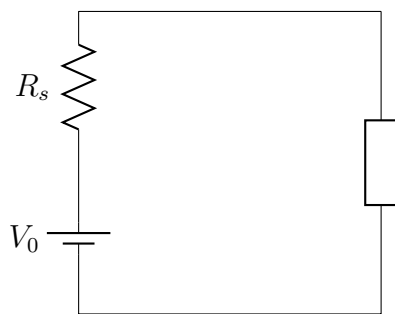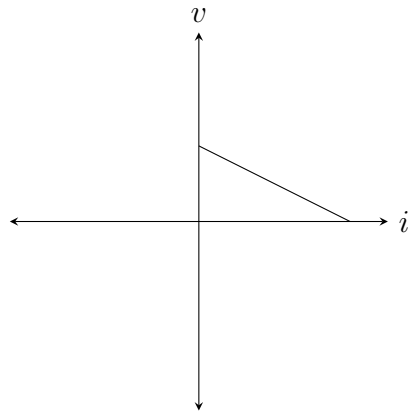

$$\begin{aligned} 0 &= -V_0 + v_R + v \\ v &= V_0 - v_R \\ \therefore v &= V_0 - R_s i \end{aligned}$$

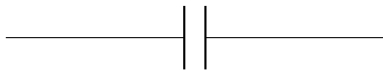3.3 Capacitor

Definition 8 (Capacitor). A capacitor is a two terminal device where V is a function of q .



3.3.1 Linear Capacitors


If the charges on the terminals of a capacitor are $+q$ and $-q$, and the potential difference across it is v , the ratio between q and v is said to be the capacitance.

The unit of capacitance is farad or F.


$$q = Cv$$

$$\therefore i = C \frac{dv}{dt}$$
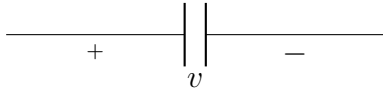
$$\therefore v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(t) dt$$



3.4 Inductor

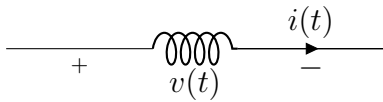

Definition 9 (Inductor).


$$v(t) = \frac{d\varphi}{dt}$$

$$\therefore v(t) = L \frac{di}{dt}$$


$$\therefore i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(t) dt$$

4 Waveforms


4.1 DC (Constant Function)

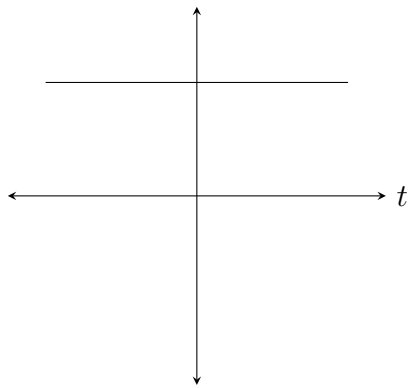

4.2 Sinusoidal Wave

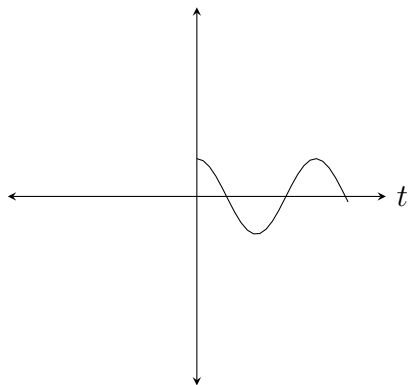


4.3 Step Function

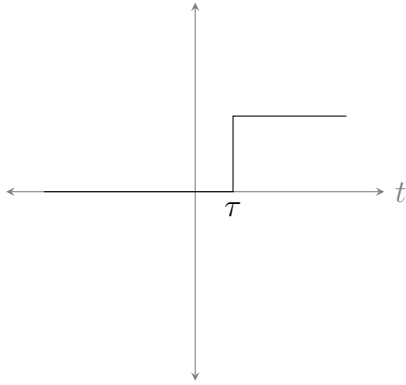

$$u(t) = \begin{cases} 0 & ; \quad t < 0 \\ \frac{1}{2} & ; \quad t = \tau \\ 1 & ; \quad t > \tau \end{cases}$$

4.4 Rectangular Pulse

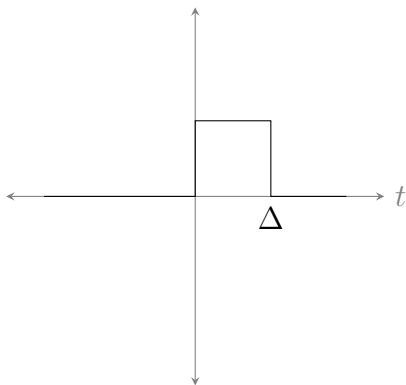

$$P_{\Delta}(t) = \frac{u(t) - u(t - \Delta)}{\Delta}$$

$$P_{\Delta}(t) = \begin{cases} 0 & ; \quad t < 0 \\ \frac{1}{\Delta} & ; \quad t = 0 \\ 1 & ; \quad t > 0 \end{cases}$$

4.5 Dirac δ function

$$\delta(t) = \lim_{\Delta \rightarrow 0} P_{\Delta}(t)$$

$$S(\Delta) = \int_{-\infty}^{\infty} P_{\Delta}(t) f(t) dt$$


As $\Delta \rightarrow 0$,

$$\begin{aligned} S(\Delta) &= \int_{-\infty}^{\infty} P_{\Delta}(t) f(0) dt \\ &= f(0) \int_{-\infty}^{\infty} P_0(t) dt \\ &= f(0) \end{aligned}$$

$$\delta(t) = \begin{cases} 0 & ; \quad t \neq 0 \\ \infty & ; \quad t = 0 \end{cases}$$

$$\begin{aligned} \int_{-\infty}^{\infty} \delta(t) f(t) dt &= f(0) \\ \int_{-\infty}^{\infty} \delta(t - \tau) f(t) dt &= f(\tau) \\ \int_{-\infty}^{\infty} \delta(at) f(t) dt &= \frac{1}{|a|} \delta(t) \end{aligned}$$

4.6 Ramp Function

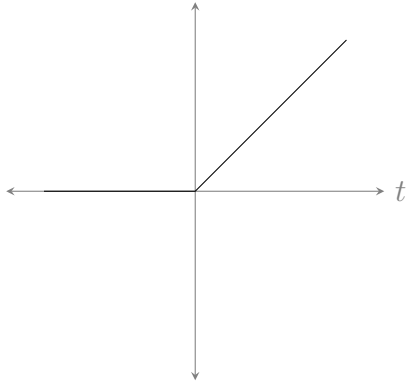

$$r(t) = tu(t)$$

4.7 Doublet Function


$$\delta'(t) = \frac{d\delta(t)}{dt}$$

4.8 Relation Between Standard Waveforms

$$r(t) \xleftrightarrow[\int_{-\infty}^t]{\frac{d}{dt}} u(t) \xleftrightarrow[\int_{-\infty}^t]{\frac{d}{dt}} \delta(t) \xleftrightarrow[\int_{-\infty}^t]{\frac{d}{dt}} \delta'(t)$$

Exercise 1.

Express the following wave as a sum of standard waveforms.

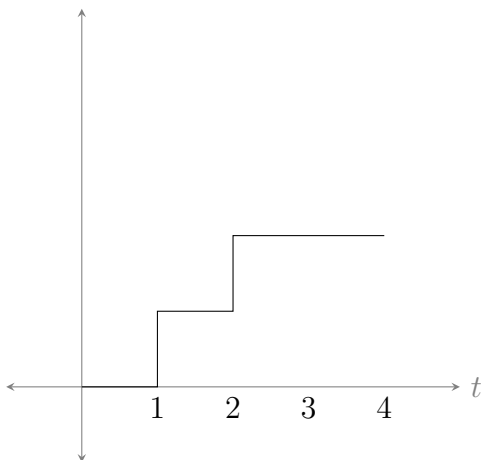


Solution 1.

$$f(t) = u(t - 1) + u(t - 2)$$

Exercise 2.

Express the following wave as a sum of standard waveforms.

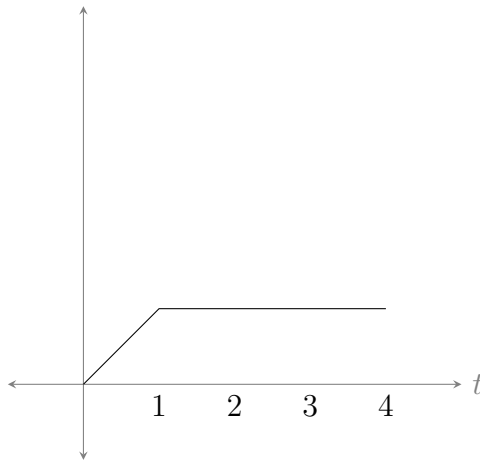

Solution 2.

$$f(t) = r(t) + r(t - 1)$$

5 Power and Energy

The instantaneous power supplied to a load is

$$P(t) = v(t) \cdot i(t)$$

where $v(t)$ and $i(t)$ are in matched directions.

The energy supplied to a load from time t_0 to time t is

$$\begin{aligned} W(t_0, t) &= \int_{t_0}^t P(t) \, dt \\ &= \int_{t_0}^t v(t) \cdot i(t) \, dt \end{aligned}$$

5.1 Energy Stored in a Capacitor

$$W(t_0, t) = \int_{t_0}^t v(t)i(t) \, dt$$

As $i(t) = \frac{dq}{dt}$, $dq = i(t) \, dt$. Therefore,

$$\begin{aligned} W(t_0, t) &= \int_{q(t_0)}^{q(t)} v(q) \, dq \\ &= \int_{q(t_0)}^{q(t)} \frac{q}{C} \, dq \\ &= \frac{q^2}{2C} \\ &= \frac{1}{2}cv^2 \end{aligned}$$

5.2 Energy Stored in an Inductor

$$W(t_0, t) = \int_{t_0}^t v(t)i(t) \, dt$$

As $v(t) = \frac{d\varphi}{dt}$, $d\varphi = v(t) \, dt$. Therefore,


$$\begin{aligned} W(t_0, t) &= \int_{\varphi(t_0)}^{\varphi(t)} i(\varphi) \, d\varphi \\ &= \frac{\varphi^2}{2L} \\ &= \frac{1}{2}Li^2 \end{aligned}$$

Part II

Simple Circuits

1 Equivalent Circuits

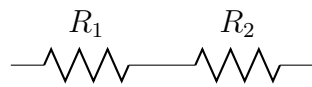Definition 10. Two circuits are said to be equivalent if they have the same $v(t)$ - $i(t)$ relationships.



Let the voltage across R_1 be v_1 and across R_2 be v_2 .
Let the current through R_1 be i_1 and through R_2 be i_2 .
Therefore,

$$v_1 = f_1(i_1)$$

$$v_2 = f_2(i_2)$$

Therefore,

$$\begin{aligned} v &= v_1 + v_2 \\ &= f_1(i_1) + f_2(i_2) \\ &= f_1(i) + f_2(i) \\ &= f_3(i) \end{aligned}$$

Therefore, the system of resistors is equivalent to a single resistor R_3 .